

AN-1381 LM3475 Evaluation Board

1 Introduction

The LM3475 evaluation board is provided as a tool for developing DC/DC converters based on the LM3475 IC. As shown in Figure 1, the evaluation board is configured to provide an output of 2.5 V at up to 2A from an input up to 10 V. The corresponding bill of material is given in Table 1. Typical efficiencies are shown in Figure 2 and Figure 3. Figure 4 and Figure 5 show the board layout.

To aid in the design and evaluation of dc/dc buck converters based on the LM3475 controller, the LM3475 Evaluation Board can be easily re-configured for different output voltages.

2 Setting Vout

$$V_{out}$$
 can be set using R_{FB1} , as shown in Equation 1:
 $V_{OUT} = V_{FB} \times (R_{FB1} + R_{FB2}) / R_{FB2}$ (1)

Where V_{FB} is 0.8 V typically.

See the device-specific data sheet before changing any component values, since additional design adjustments may be required.

3 Optional Components

A feed-forward capacitor C_{FF} is placed on the board, which will increase operating frequency. However, the speed up effect decreases with lower output voltage and is negligible below 1.6 V output.

A zero Ohm is used to pull up the EN pin for always on operation. The enable pin can be pulled low at the EN post to shutdown the device. If this resistor is removed, any analog level signal can be used to enable and disable the device.

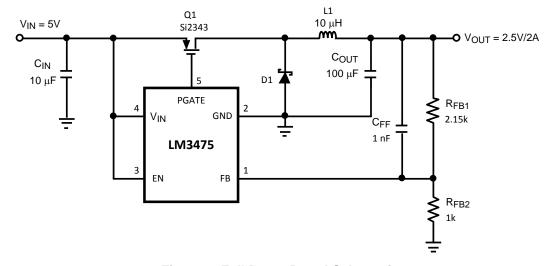


Figure 1. Full Demo Board Schematic

All trademarks are the property of their respective owners.



Optional Components www.ti.com

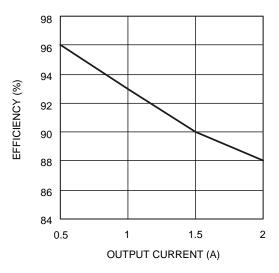


Figure 2. Efficiency vs Output Current $(V_{IN} = 5 V)$

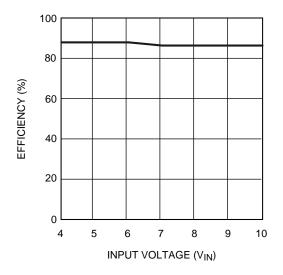


Figure 3. Efficiency vs Input Voltage ($I_{out} = 2A$)

Table 1. Bill of Materials (BOM)

Part Description

| Designator | Part Description | Part Number |
|------------|---------------------|----------------------|
| CIN | 10 μF 16 V ceramic | Yuden EMK325BJ106MN |
| COUT | 100 μF 6 V tantalum | AVX TPSY107M006R0100 |
| CFF | 1 nF 25 V ceramic | VJ1206Y102KXXA |
| D1 | Schottky 20 V 2A | Central CMSH2-20L |
| L1 | 10 μH 3.1 A | Sumida CDRH103R100 |
| Q1 | Si 2343 30 V 2.5A | Vishay Si2343 |
| RFB2 | 1 kΩ | Vishay CRCW08051001F |
| RFB1 | 2.15 kΩ | Vishay CRCW08052151F |
| R2 | 0 Ω | Vishay CRCW08050R00F |



4 PCB Layout Diagram(s)

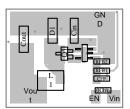


Figure 4. Top Side Layout



Figure 5. Bottom Side Layout

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have *not* been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products Applications

Audio www.ti.com/audio Automotive and Transportation www.ti.com/automotive Communications and Telecom **Amplifiers** amplifier.ti.com www.ti.com/communications **Data Converters** dataconverter.ti.com Computers and Peripherals www.ti.com/computers **DLP® Products** www.dlp.com Consumer Electronics www.ti.com/consumer-apps

DSP **Energy and Lighting** dsp.ti.com www.ti.com/energy Clocks and Timers www.ti.com/clocks Industrial www.ti.com/industrial Interface interface.ti.com Medical www.ti.com/medical logic.ti.com Logic Security www.ti.com/security

Power Mgmt power.ti.com Space, Avionics and Defense www.ti.com/space-avionics-defense

Microcontrollers microcontroller.ti.com Video and Imaging www.ti.com/video

RFID <u>www.ti-rfid.com</u>

OMAP Applications Processors www.ti.com/omap TI E2E Community e2e.ti.com

Wireless Connectivity <u>www.ti.com/wirelessconnectivity</u>