

- 1mA Quiescent Current
- 50mA Output Current (Minimum)
- 10MHz Bandwidth
- 500V/us Slew Rate
- 280ns Settling Time to 0.1%
- Wide Supply Range, $±5V$ to $±15V$
- 1mV Input Offset Voltage
- 100nA Input Bias Current
- 100MΩ Input Resistance

U A S O PPLICATI

- Video Amplifiers
- Buffers
- IF and RF Amplification
- Cable Drivers

 \boldsymbol{I} \boldsymbol{I} little

■ 8, 10, 12-Bit Data Acquisition Systems

Low Power 10MHz Current Feedback Amplifier

D ^U FEATURES ESCRIPTIO

The LT1217 is a 10MHz current feedback amplifier with DC characteristics better than many voltage feedback amplifiers. This versatile amplifier is fast, 280ns settling to 0.1% for a 10V step thanks to its 500V/µs slew rate. The LT1217 is manufactured on Linear Technology's proprietary complementary bipolar process resulting in a low 1mA quiescent current. To reduce power dissipation further, the LT1217 can be turned off, eliminating the load current and dropping the supply current to 350µA.

The LT1217 is excellent for driving cables and other low impedance loads thanks to a minimum output drive current of 50mA. Operating on any supplies from \pm 5V to \pm 15V allows the LT1217 to be used in almost any system. Like other current feedback amplifiers, the LT1217 has high gain bandwidth at high gains. The bandwidth is over 1MHz at a gain of 100.

The LT1217 comes in the industry standard pinout and can upgrade the performance of many older products.

TYPICAL APPLICATION

Cable Driver Cable Oriental Cable Driver Cable Driver Cable Driver Cable Driver Cable Oriental Cable Driver Cable Oriental Cable Or

1

ABSOLUTE MAXIMUM RATINGS PACKAGE/ORDER INFORMATION

ELECTRICAL CHARACTERISTICS $V_S = \pm 15V$, $T_A = 0^\circ C$ to 70 $^\circ C$ unless otherwise noted.

The ● denotes specifications which apply over the operating temperature range.

Note 1: A heat sink may be required.

Note 2: Non-Inverting operation, $V_{OUT} = \pm 10V$, measured at $\pm 5V$.

Note 3: AC parameters are 100% tested on the plastic DIP packaged parts (N suffix), and are sample tested on every lot of the SO packaged parts (S suffix).

C C HARA TERISTICS U W TYPICAL PERFOR A CE

C C HARA TERISTICS U W TYPICAL PERFOR A CE

FREQUENCY (MHz)

 $V_S = \pm 15V$ NEGATIVE

 $R_L = 100Ω$ $R_F = R_G = 3k$ POSITIVE

0.1 1 10

LT1217 • TPC17

 0.01 0

20

30 40

10

50 60 70

POWER SUPPLY REJECTION (dB)

POWER SUPPLY REJECTION (dB)

Input Common Mode Limit vs Output Saturation Voltage vs Output Short Circuit Current vs

10000 \Box

Settling Time to 10mV vs

Output Step

Output Step **Supply Current vs Supply Voltage** 10 10 1.4 \mathbf{I} $V_S = \pm 15V$ $V_S = \pm 15V$ 8 8 $T = 125^{\circ}$ C $R_F = R_G = 3k$ 1.2 $R_F = R_G = 3k$ 6 6 INVERTING SUPPLY CURRENT (mA) SUPPLY CURRENT (mA 1.0 4 4 NON-INVERTING $= 25^{\circ}$ C \odot OUTPUT STEP (V) OUTPUT STEP (V) OUTPUT STEP (V) INVERTING 2 2 **OUTPUT STEP** NON-INVERTING 0.8 $T = -55^{\circ}C$ $\overline{0}$ 0 0.6 NON-INVERTING –2 –2 $T = -55^{\circ}C$ NON-INVERTING $= 25^{\circ}$ C, 125 $^{\circ}$ C –4 –4 0.4 –6 –6 SHUTDOWN-0.2 INVERTING –8 –8 PIN 8 AT GND **INVERTING** –10 –10 0.0 100 0 50 100 150 200 250 300 0 300 $\overline{0}$ 200 400 500 2 4 6 8 10 12 14 16 18 SUPPLY VOLTAGE (±V) SETTLING TIME (ns) SETTLING TIME (ns) LT1217 • TPC19 LT1217 • TPC20 LT1217 • TPC21

C C HARA TERISTICS U W TYPICAL PERFOR A CE

U A S O PPLICATI W U U I FOR ATIO

Current Feedback Basics

The small signal bandwidth of the LT1217, like all current feedback amplifiers, isn't a straight inverse function of the closed loop gain. This is because the feedback resistors determine the amount of current driving the amplifier's internal compensation capacitor. In fact, the amplifier's feedback resistor (R_F) from output to inverting input works with internal junction capacitances of the LT1217 to set the closed loop bandwidth.

Even though the gain set resistor (R_G) from inverting input to ground works with R_F to set the voltage gain just like it does in a voltage feedback op amp, the closed loop bandwidth does not change. This is because the equivalent gain bandwidth product of the current feedback amplifier is set by the Thevenin equivalent resistance at the inverting input and the internal compensation capacitor. By keeping R_F constant and changing the gain with R_G , the Thevenin resistance changes by the same amount as the change in gain. As a result, the net closed loop bandwidth of the LT1217 remains the same for various closed loop gains.

The curve on the first page shows the LT1217 voltage gain versus frequency while driving 100Ω, for five gain settings from 1 to 100. The feedback resistor is a constant 3k and the gain resistor is varied from infinity to 30Ω. Second order effects reduce the bandwidth somewhat at the higher gain settings.

Feedback Resistor Selection

The small signal bandwidth of the LT1217 is set by the external feedback resistors and the internal junction capacitors. As a result, the bandwidth is a function of the supply voltage, the value of the feedback resistor, the closed loop gain and load resistor. The characteristic curves of bandwidth versus supply voltage are done with a heavy load (100 Ω) and a light load (1k Ω) to show the effect of loading. These graphs also show the family of curves that result from various values of the feedback resistor. These curves use a solid line when the response has less than 0.5dB of peaking and a dashed line when the response has 0.5dB to 5dB of peaking. The curves stop where the response has more than 5dB of peaking.

At a gain of two, on $\pm 15V$ supplies with a 3k Ω feedback resistor, the bandwidth into a light load is 13.5MHz with a little peaking, but into a heavy load the bandwidth is 10MHz with no peaking. At very high closed loop gains, the bandwidth is limited by the gain bandwidth product of about 100MHz. The curves show that the bandwidth at a closed loop gain of 100 is about 1MHz.

Capacitance on the Inverting Input

Current feedback amplifiers want resistive feedback from the output to the inverting input for stable operation. Take

U A S O PPLICATI W U U I FOR ATIO

care to minimize the stray capacitance between the output and the inverting input. Capacitance on the inverting input to ground will cause peaking in the frequency response (and overshoot in the transient response), but it does not degrade the stability of the amplifier. The amount of capacitance that is necessary to cause peaking is a function of the closed loop gain taken.

The higher the gain, the more capacitance is required to cause peaking. We can add capacitance from the inverting input to ground to increase the bandwidth in high gain applications. For example, in this gain of 100 application, the bandwidth can be increased from 1MHz to 2MHz by adding a 2200pF capacitor.

Boosting Bandwidth of High Gain Amplifier with Capacitance on Inverting Input

Capacitive Loads

The LT1217 can be isolated from capacitive loads with a small resistor (10 Ω to 20 Ω) or it can drive the capacitive load directly if the feedback resistor is increased. Both techniques lower the amplifier's bandwidth about the same amount. The advantage of resistive isolation is that the bandwidth is only reduced when the capacitive load is present. The disadvantage of resistor isolation is that resistive loading causes gain errors. Because the DC accuracy is not degraded with resistive loading, the desired way of driving capacitive loads, such as flash converters, is to increase the feedback resistor. The Maximum Capacitive Load versus Feedback Resistor curve shows the value of feedback resistor and capacitive load that gives 5dB of peaking. For less peaking, use a larger feedback resistor.

Power Supplies

The LT1217 may be operated with single or split supplies as low as $\pm 4.5V$ (9V total) to as high as $\pm 18V$ (36V total). It is not necessary to use equal value split supplies, however, the offset voltage will degrade about 350µV per volt of mismatch. The internal compensation capacitor decreases with increasing supply voltage. The –3dB Bandwidth versus Supply Voltage curves show how this affects the bandwidth for various feedback resistors. Generally, the bandwidth at $\pm 5V$ supplies is about half the value it is at \pm 15V supplies for a given feedback resistor.

The LT1217 is very stable even with minimal supply bypassing, however, the transient response will suffer if the supply rings. It is recommended for good slew rate and settling time that 4.7μ F tantalum capacitors be placed within 0.5 inches of the supply pins.

Input Range

The non-inverting input of the LT1217 looks like a 100M Ω resistor in parallel with a 3pF capacitor until the common mode range is exceeded. The input impedance drops somewhat and the input current rises to about 10µA when the input comes too close to the supplies. Eventually, when the input exceeds the supply by one diode drop, the base collector junction of the input transistor forward biases and the input current rises dramatically. The input current should be limited to 10mA when exceeding the supplies. The amplifier will recover quickly when the input is returned to its normal common mode range unless the input was over 500mV beyond the supplies, then it will take an extra 100ns.

^U A S O PPLICATI ^W ^U ^U I FOR ATIO

Offset Adjust

Output offset voltage is equal to the input offset voltage times the gain plus the inverting input bias current times the feedback resistor. The LT1217 output offset voltage can be nulled by pulling approximately 30µA from pin 1 or 5. The easy way to do this is to use a 100k Ω pot between pin 1 and 5 with a 430k Ω resistor from the wiper to ground for 15V supply applications. Use a 110k resistor when operating on a 5V supply.

Shutdown

Pin 8 activates a shutdown control function. Pulling more than 50µA from pin 8 drops the supply current to less than 350µA, and puts the output into a high impedance state. The easy way to force shutdown is to ground pin 8, using an open collector (drain) logic stage. An internal resistor limits current, allowing direct interfacing with no additional parts. When pin 8 is open, the LT1217 operates normally.

Slew Rate

The slew rate of a current feedback amplifier is not independent of the amplifier gain configuration the way it is in a traditional op amp. This is because the input stage and the output stage both have slew rate limitations. Inverting amplifiers do not slew the input and are therefore limited only by the output stage. High gain, non-inverting amplifiers are similar. The input stage slew rate of the LT1217 is about 50V/us before it becomes non-linear and is enhanced by the normally reverse biased emitters on the input transistors. The output slew rate depends on the size of the feedback resistors. The output slew rate is about 850V/µs with a 3k feedback resistor and drops proportionally for larger values. The photos show the LT1217 with a 20V peak-to-peak output swing for three different gain configurations.

Settling Time

The characteristic curves show that the LT1217 settles to within 10mV of final value in less than 300ns for any output step up to 10V. Settling to 1mV of final value takes less than 500ns.

Large Signal Response, $A_V = 2$, $R_F = R_G = 3k$, **Slew Rate** \simeq 500V/ μ **s**

Large Signal Response, $A_V = -2$ **,** $B_F = 3k$ **,** $B_G = 1.5k$ **, Slew Rate** $\simeq 850V/\mu s$

Large Signal Response, $A_V = 10$, $R_F = 3k$, $R_G = 330\Omega$, **Slew Rate** \simeq **150V/** μ **s**

S **IMPLIFIED SCHEMATIC**

Dimensions in inches (millimeters) unless otherwise noted. ^U PACKAGE DESCRIPTIO

Mouser Electronics

Authorized Distributor

Click to View Pricing, Inventory, Delivery & Lifecycle Information:

[Analog Devices Inc.](https://www.mouser.com/linear-technology):

[LT1217CS8#TR](https://www.mouser.com/access/?pn=LT1217CS8#TR) [LT1217CN8#PBF](https://www.mouser.com/access/?pn=LT1217CN8#PBF) [LT1217CS8](https://www.mouser.com/access/?pn=LT1217CS8) [LT1217CS8#TRPBF](https://www.mouser.com/access/?pn=LT1217CS8#TRPBF) [LT1217CN8](https://www.mouser.com/access/?pn=LT1217CN8) [LT1217CS8#PBF](https://www.mouser.com/access/?pn=LT1217CS8#PBF)